

LC Time Interpretation

Benjamin Bauml

Winter 2024

This problem is borrowed from Chapter 30 of the *Student Workbook for Physics for Scientists and Engineers*.

Activity

The capacitor in an LC circuit has maximum charge at $t = 1 \text{ }\mu\text{s}$. The current through the inductor next reaches a maximum at $t = 3 \text{ }\mu\text{s}$.

(a) When will the inductor current reach a maximum in the opposite direction?

The current in an LC circuit oscillates as $I = I_{max} \sin(\omega t + \phi)$, where ϕ is some phase constant. The charge on the capacitor is maximum when the current is zero, so the two events are 90° out of phase. That means the time between the two is a quarter of the circuit's period:

$$\Delta t = 2 \text{ }\mu\text{s} = \frac{T}{4}.$$

The inductor current changes direction after a 180° phase change, so we need to add half of the period ($T/2 = 4 \text{ }\mu\text{s}$) to the time of the first maximum ($t = 3 \text{ }\mu\text{s}$) to reach the inverted maximum. That gives us the desired time of $t = 7 \text{ }\mu\text{s}$.

(b) What is the circuit's period of oscillation?

As we said before, $\Delta t = \frac{T}{4}$, so $T = 8 \text{ }\mu\text{s}$.