

PH 223 Week 6

Benjamin Bauml

Winter 2024

The first two problems are adapted from Grant Sherer. The final problem is adapted from Chapter 28 of the *Student Workbook for Physics for Scientists and Engineers*.

Activity 1

Three $45\ \Omega$ resistors are in parallel, connected to a $21\ \Omega$ resistor in series with a battery of potential difference $9\ \text{V}$.

- (a) Draw a diagram of the circuit and a voltage diagram for at least one loop.
- (b) Write loop and junction rules that completely characterize the circuit. (Use each resistor in at least 1 loop rule and 1 junction rule.)
- (c) Find R_{eq} .

Activity 2

Sketch a circuit that uses any number of $12\ \Omega$ resistors to create an equivalent resistance of:

- (a) $60\ \Omega$
- (b) $3\ \Omega$
- (c) $10\ \Omega$

Activity 3

(a) Draw a circuit for which the Kirchhoff's loop law equation is

$$6 \text{ V} - I \cdot 2 \, \Omega + 3 \text{ V} - I \cdot 4 \, \Omega = 0.$$

Assume that the analysis is done in a clockwise direction.

(b) A voltage diagram is shown below for a different circuit. The current in the circuit is 2.0 A. Draw the circuit diagram and identify the points on the circuit diagram that are on the voltage diagram.

